


## EXPERIMENT-6

### Measurement of Capacitance by Schering Bridge

#### Objective

- To Determine the Capacitance of an unknown Capacitor.

#### Theory

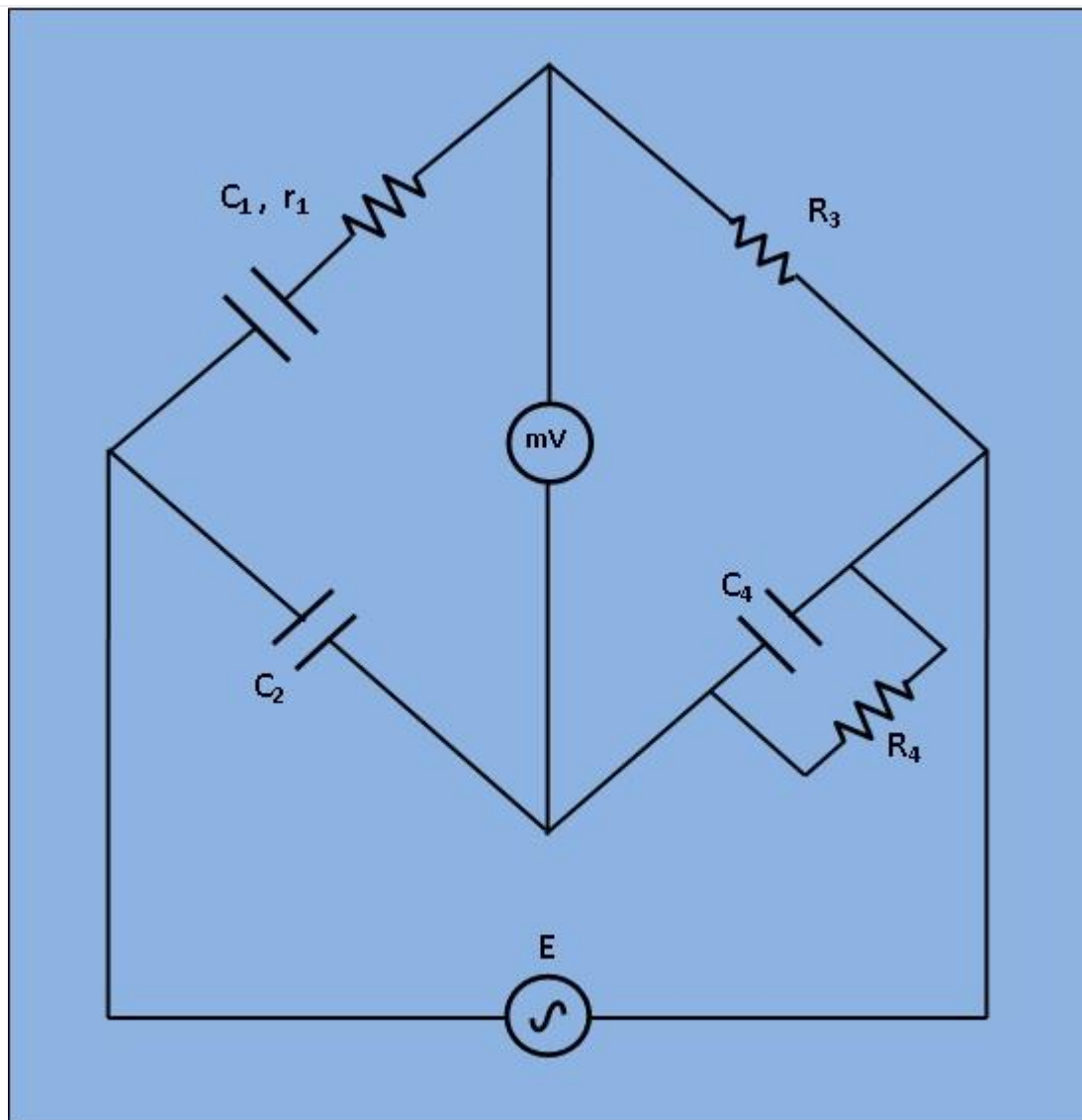

- **Fig 1: Circuit diagram for measurement of Capacitance by Schering Bridge**

- Let,
- $C_1$ =capacitor whose capacitance is to be measured.
- $r_1$ = a series resistance representing the loss in the capacitor  $C_1$ .
- $C_2$ = a standard capacitor.
- $R_3$ = a non inductive resistance.
- $C_4$ = a variable capacitor.
- $R_4$ = a variable non inductive resistance.
- At balance,

$$(r_1 + \frac{1}{j\omega C_1}) * (\frac{R_4}{j\omega C_4 R_4 + 1}) = \frac{R_3}{j\omega C_2} \dots\dots (1)$$

$$r_1 R_4 - \frac{jR_4}{\omega C_1} = -\frac{jR_3}{\omega C_2} + \frac{R_3 R_4 C_4}{C_2} \dots\dots (2)$$

Or Equating the real and imaginary terms in equa. (2), we obtain

$$r_1 = R_3 * \frac{C_4}{C_2} \dots\dots (3)$$


$$C_1 = R_4 * \frac{C_2}{R_3} \dots\dots (4)$$

And, Two independent balance equations (3) and (4) are obtained if  $C_4$  and  $R_4$  are chosen as the variable elements.

Dissipation factor

$$D_1 = \omega C_1 r_1 \dots (5)$$

## Procedure

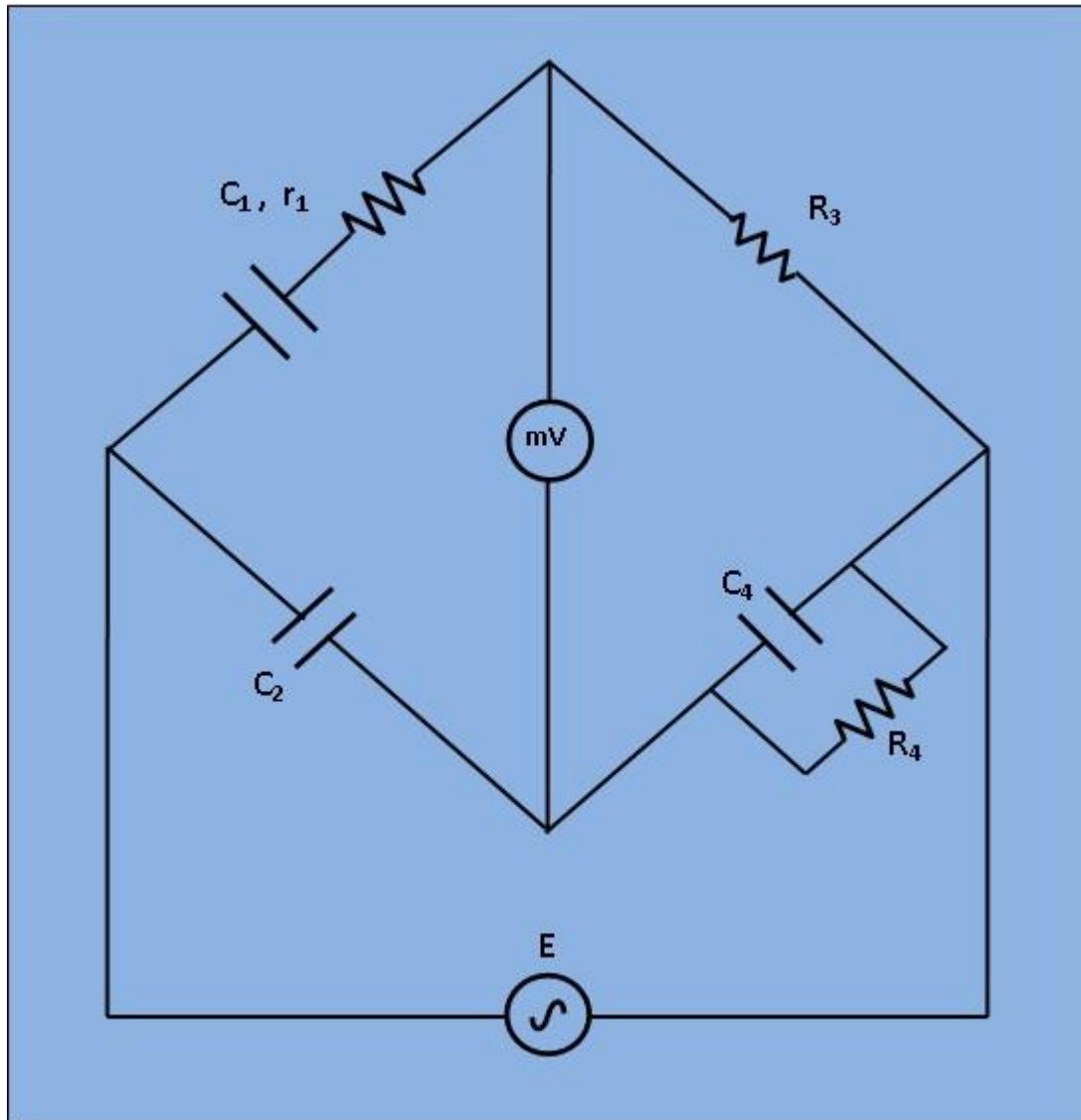


**Fig. 1. Circuit diagram of experimental set-up for Capacitance measurement by Schering Bridge.**

- 1) Apply Supply voltage from the signal generator with arbitrary frequency. (  $V = 3V$  ). Also set the unknown Capacitance value from 'Set Capacitor Value' tab.

- 2) Then switch on the supply to get millivoltmeter deflection.
- 3) Choose the values of  $C_2$ ,  $C_4$ ,  $R_3$  and  $R_4$  from the capacitance and resistance box. Vary the values to some particular values to achieve "NULL".
- 4) Observe the millivoltmeter pointer to achieve "NULL".
- 5) If "NULL" is achieved, switch to 'Measure Capacitor Value' tab and click on 'Simulate'. Observe the calculated values of unknown capacitance ( $C_1$ ) and its internal resistance ( $r_1$ ).
- 6) Also observe the Dissipation factor of the unknown capacitor which is defined as

$$\omega * C * r \text{ Where, } \omega = 2\pi f$$

Simulation :

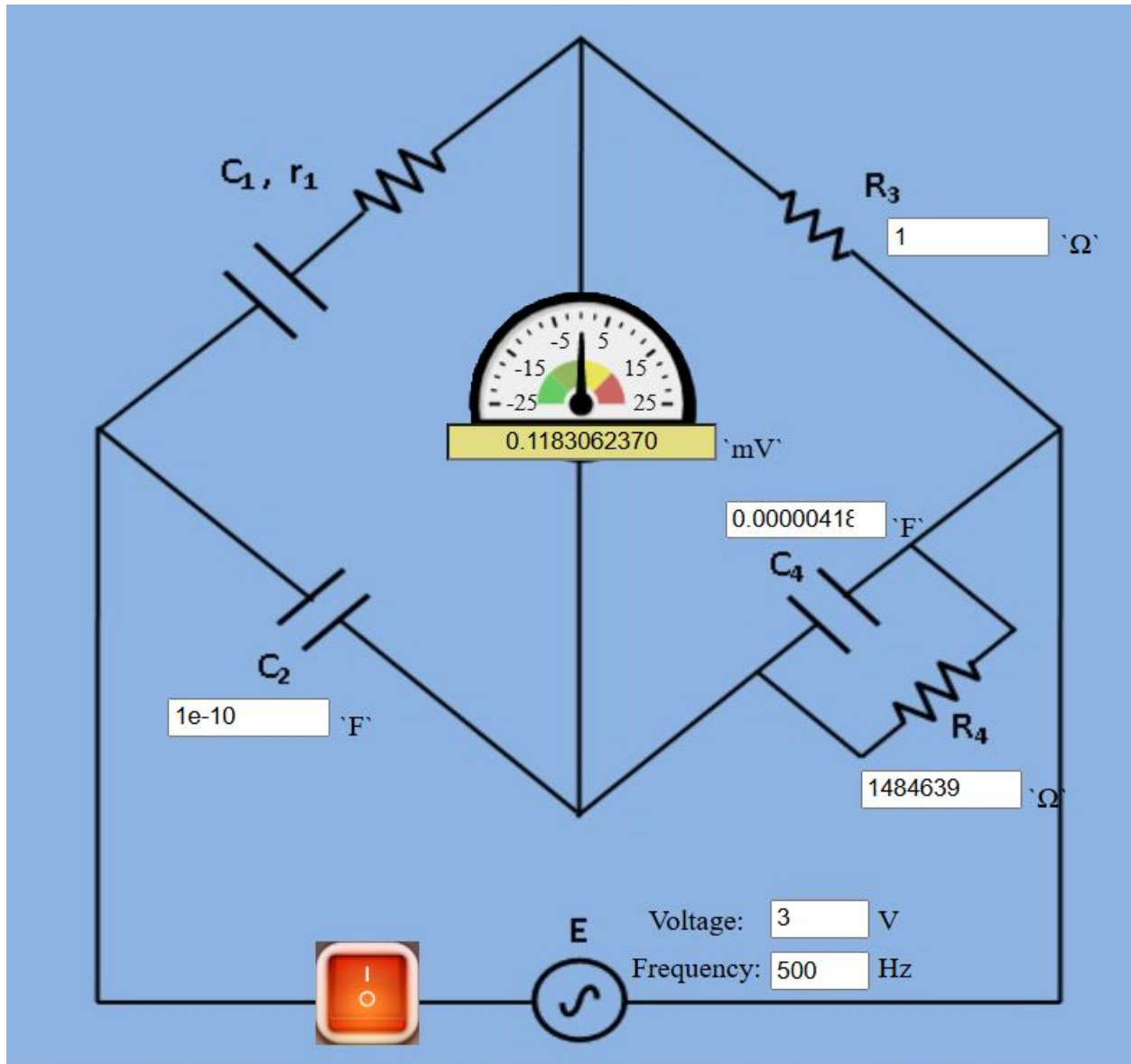

The current voltmeter reading is:  $0.1183062370$  mv. Now simulate to get:

Capacitor value (in uF):  $148.46$

Resistance value (in  $\Omega$ ):  $41898$

Dissipation Factor:  $19532$

Simulate

#### CONTROLS

R3 : $1 \Omega$	<input type="range"/>	11.1111 M $\Omega$
R4 : $1 \Omega$	<input type="range"/>	11.1111 M $\Omega$
C2 : 100 pF	<input type="range"/>	11.111uF
C4 : 100 pF	<input type="range"/>	11.111uF

Result:

Thus the measurement of capacitance by Schering Bridge is simulated and validated.